

State-of-the-Art in Equivalence Checking

Wolfgang Kunz
University of Kaiserslautern, Germany

Slide 1

Overview

Verification gap:

SIA Roadmap: 60% of design resources are consumed by verification!


Formal methods – the answer?

- what tools exist?
- what is the underlying technology?
- equivalence checking and property checking

Slide 2

Background

Typical design flow using a standard synthesis tool

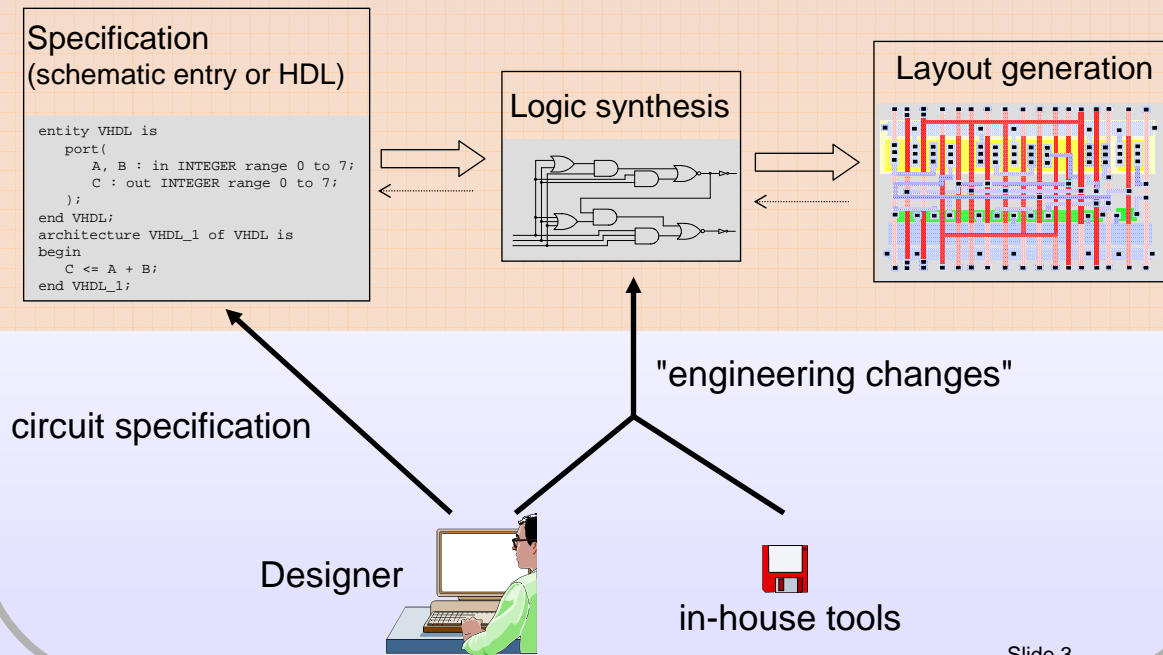

Slide 3

Task of Verification

1. Does the formal specification fulfill the expectations of the designer?

- can unexpected situations occur? (e.g.: deadlocks)
- are there unexpected side effects?
- do certain things always work?

"design verification"

Verification method: *"property checking"* or *"model checking"*

Slide 4

Task of Verification

2. Has the specification been correctly translated into an implementation?

error sources:

- bugs in synthesis tool
- problems with interfacing several tools
- manual interaction of the designer

"implementation verification"

Verification method: *"equivalence checking"*

Slide 5

Industrial Practice

Implementation verification: *equivalence checking*

mostly based on SAT, ATPG and local BDDs

usage:

- check equivalence of specification and implementation
- verify implementation repeatedly after synthesis and engineering changes,
- can be integrated into regression testing environment,
- feasible for 1,000,000 gates and more for combinational equivalence checking

Slide 6

The engines

binary decision diagrams (BDDs)

- special graph representation of Boolean function
- many problems that are difficult to solve for conventional representations of Boolean functions are easy to solve for BDDs

SAT-solving methods (SAT-solvers)

- decide whether or not a Boolean function can be 1
- many verification problems can be mapped to a SAT-problem

Slide 7

Decision diagrams (DDs)

Important contribution to handle complexity:

graph representation of Boolean functions
(OBDDs ("ordered binary decision diagrams"), [Brya86])

many types of decision diagrams:

OBDDs, FDDs, OKFDDs, IBDDs, ADDs, MTBDDs, EVBDDs,
BMDs, *BMDs, K*BMDs, PHDDs u.a.

“alphabet soup DDs“

Slide 8

Decision diagrams (DDs)

Important properties of a Boolean function representation:

- Canonicity (uniqueness)
e.g. truth table
- Compactness
e.g. multi-level netlist (Boolean network)
- easy to perform Boolean operations (AND, OR, NOT)
e.g. multi-level netlist
- easy to solve Boolean decision problems (SAT)
e.g. truth table

DDs attempt to find the ideal compromise between these requirements.

Slide 9

Decision diagrams (DDs)

for most DDs:

- directed acyclic graph with one or several root nodes
- every sub-graph rooted in some node represents a Boolean function
- every node corresponds to a decomposition of its associated function
- the terminal nodes of the graph correspond to the terminal cases of the decomposition (e.g. the output values of the function)


Slide 10

Ordered binary decision diagrams (OBDDs)

underlying decomposition: Shannon decomposition

$$y(x_1, \dots, x_n) = x_i \cdot y(x_1, \dots, x_i = 1, \dots, x_n) + \bar{x}_i \cdot y(x_1, \dots, x_i = 0, \dots, x_n)$$


$$\text{short notation: } y = x \cdot y|_{x=1} + \bar{x} \cdot y|_{x=0}$$

 

Slide 11

 Example

$$y = abc + a\bar{b}\bar{c} + \bar{a}bc + \bar{a}\bar{b}c$$




binary decision diagram (Shannon-tree) for 3-bit parity function


Slide 12

Reduction

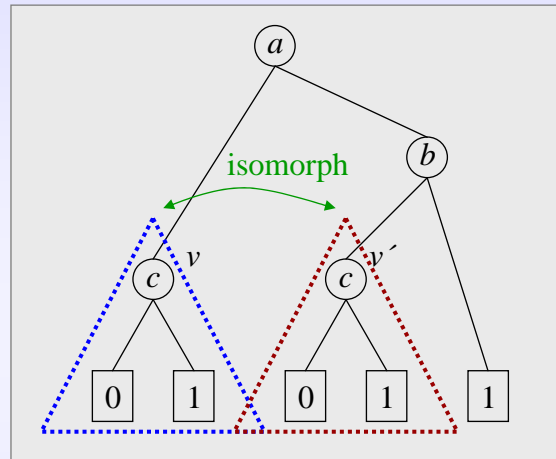- nodes with isomorphic sub-graphs can be merged




- nodes with only one immediate successor can be eliminated

 

Slide 13

Example

 

Reduced ordered binary decision diagram (ROBDD)
for 3-bit parity function

Slide 14

Canonicity

A reduced ordered binary decision diagram (ROBDD) is a canonical representation of a Boolean function.

Theorem (Bryant, 86):

Two Boolean functions are functionally equivalent if and only if their ROBDDs are isomorphic.

Slide 15

Boolean manipulation

If-Then-Else-Operator: $ite(f, g, h) = f \cdot g + \bar{f} \cdot h$
„if f then g , else h “

Every Boolean function of two variables, i.e. every binary operation can be expressed by the ite-Operator:

$$\text{e.g.: } f \cdot g = ite(f, g, 0), \quad f + g = ite(f, 1, g),$$


Let x be the “top-variable” of the ROBDD that shall be formed out of f , g , and h . It is:

$$ite(f, g, h) = ite(x, ite(f|_{x=1}, g|_{x=1}, h|_{x=1}), ite(f|_{x=0}, g|_{x=0}, h|_{x=0}))$$

Slide 16

Boolean manipulation

$$ite(f, g, h) = ite(x, ite(f|_{x=1}, g|_{x=1}, h|_{x=1}), ite(f|_{x=0}, g|_{x=0}, h|_{x=0}))$$

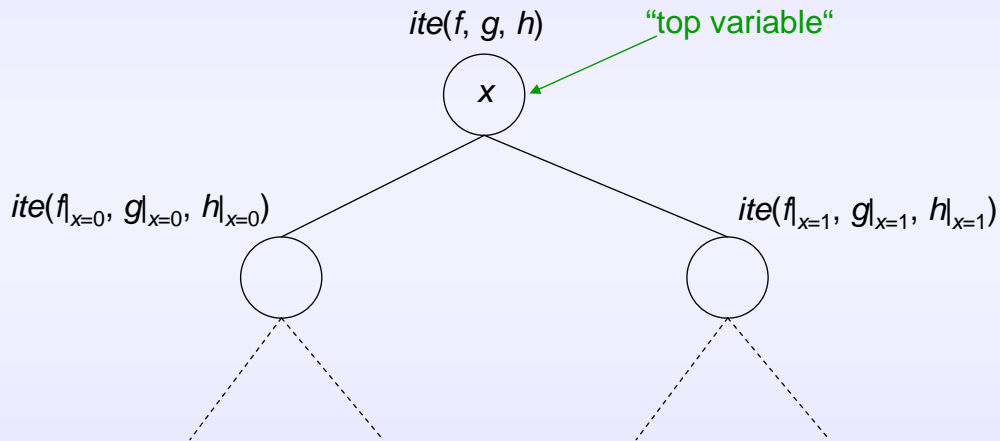

Terminal cases of recursion:

- a) $ite(1, f, g) = ite(0, g, f) = ite(f, 1, 0) = ite(g, f, f) = f$
- b) $ite(f, 0, 1) = \overline{f}$

Slide 17

Important operations

Let f be a Boolean function represented as OBDD with $|f|$ nodes:


	operation	complexity
<i>reduce</i> :	makes OBDD canonical	$O(f)$
<i>apply</i> :	$y = y(f_1, f_2)$ (beruht auf <i>ite</i> -Operator)	$O(f_1 \cdot f_2)$
<i>restrict</i> :	$f = (x_1, \dots, x_i = V, \dots, x_n)$, $V \in \{0, 1\}$	$O(f)$
<i>compose</i> :	$f_1 = (x_1, \dots, x_i = f_2, \dots, x_n)$	$O(f_1 ^2 \cdot f_2)$

Operations on OBDDs


Slide 18

Variable order

 Variable order is important for many functions!



a) $y = x_1x_2 + x_3x_4 + x_5x_6$

 

b) $y = x_1x_4 + x_2x_5 + x_3x_6$

For some functions ROBDD grows exponentially with number of variables for every variable order, e.g. multiplier.

Slide 19

OFDDs (ordered functional decision diagrams)

underlying decomposition: (positive) Reed-Muller-decomposition
(Davió-decomposition)

$$y(x_1, \dots, x_n) = y(x_1, \dots, x_i=0, \dots, x_n) \oplus x_i (y(x_1, \dots, x_i=1, \dots, x_n) \oplus y(x_1, \dots, x_i=0, \dots, x_n))$$

short notation: $y = y_{|x=0} \oplus x(y_{|x=0} \oplus y_{|x=1})$

- sometimes more compact
- Boolean manipulations have exponential worst-case complexity
- multipliers still explode

Slide 20

Equivalence Checking

given: two sequential circuit descriptions
(RTL-level or gate-level)

prove equivalence of the two designs

Combinational equivalence checking:


circuits have the same state encoding

⇒ check whether or not combinational blocks implement the same Boolean function

Only *combinational* equivalence checking is sufficiently mature for industrial use!

Slide 21

General Procedure

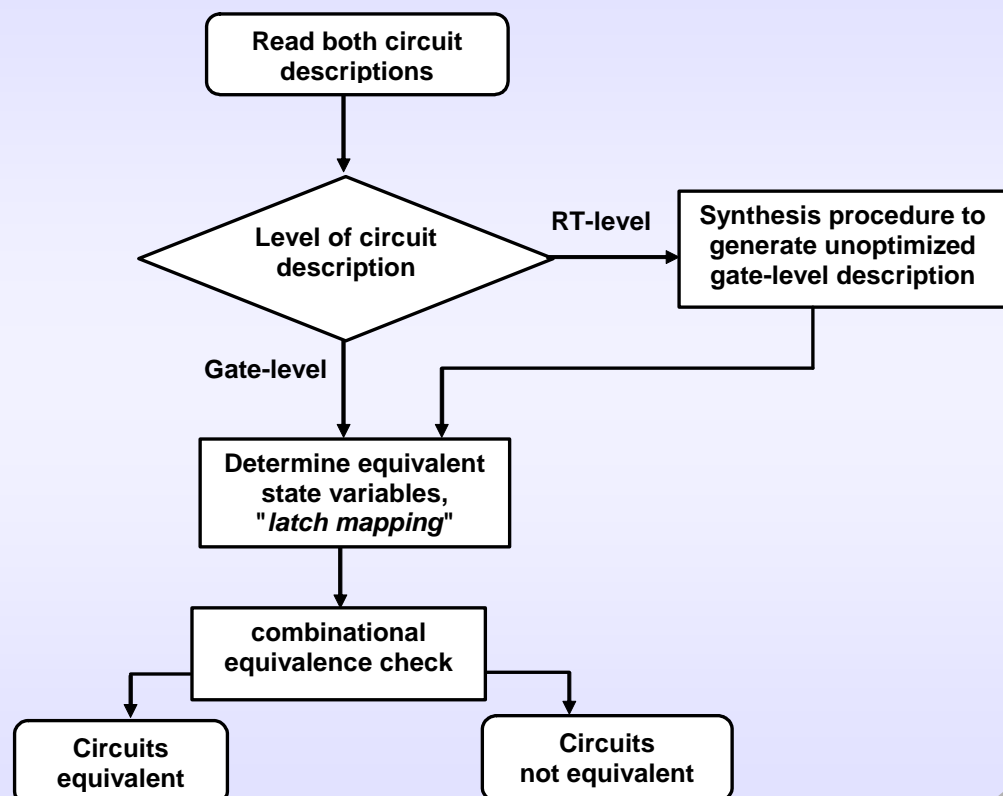

Slide 22

"Latch Mapping" or "State Matching"

Identify equivalent state variables

- manually by user interaction
- automatically by name
- automatically by function

Slide 23

State matching

Basic procedure

1. Put all state variables into one equivalence class
2. Prove non-equivalence of some state variables
3. Split equivalence class(es) accordingly

Iterate Step 2 and 3 until no further refinement is obtained.


How to prove non-equivalent state variables?

Slide 24

State matching

Example

put all state variables into one class and simulate

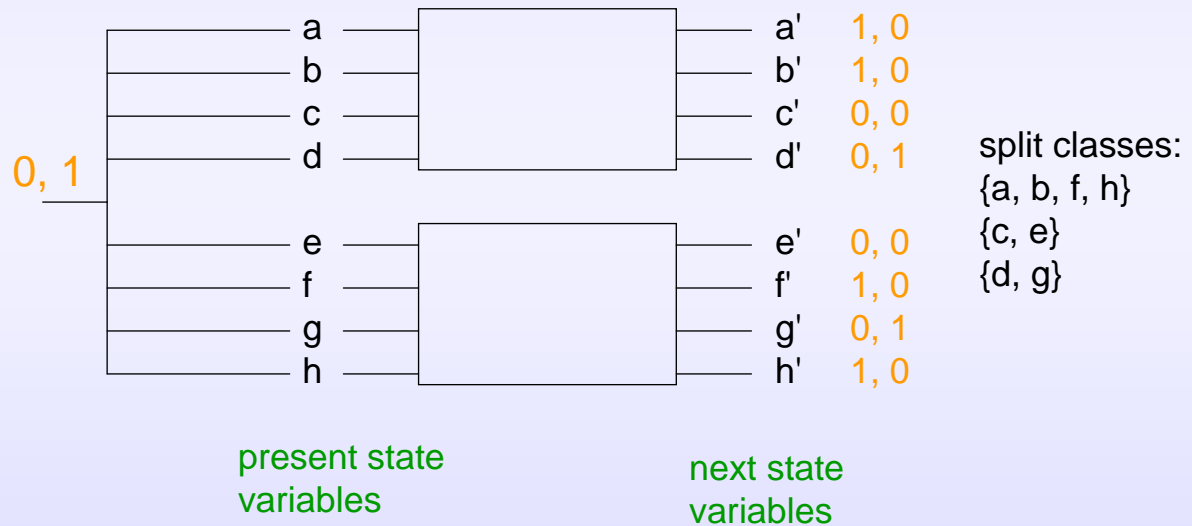


Slide 25

State matching

Example

refine equivalence class and simulate again

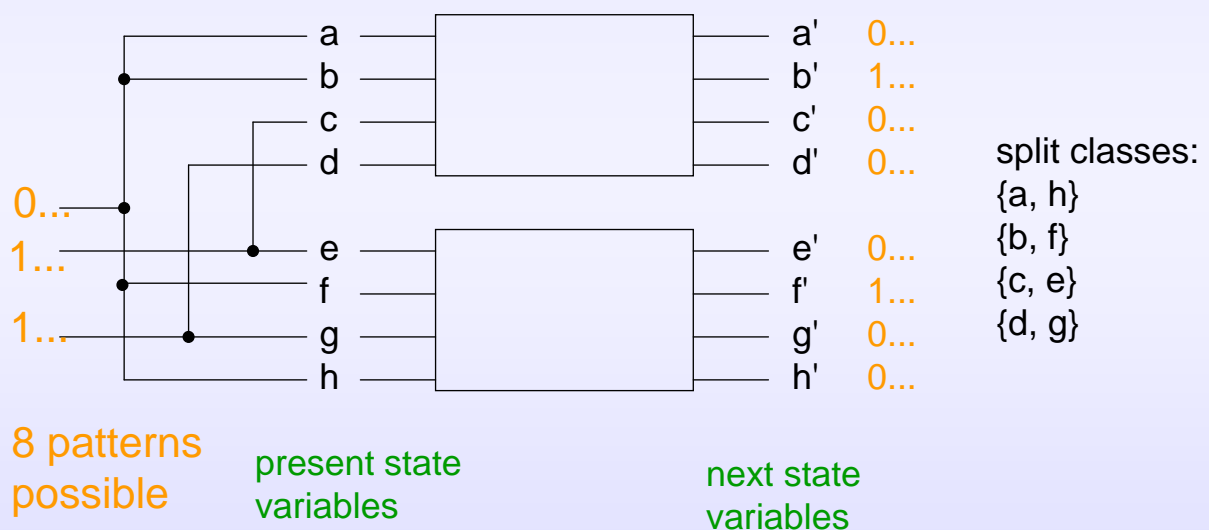


Slide 26

State matching

Example

latch mapping complete

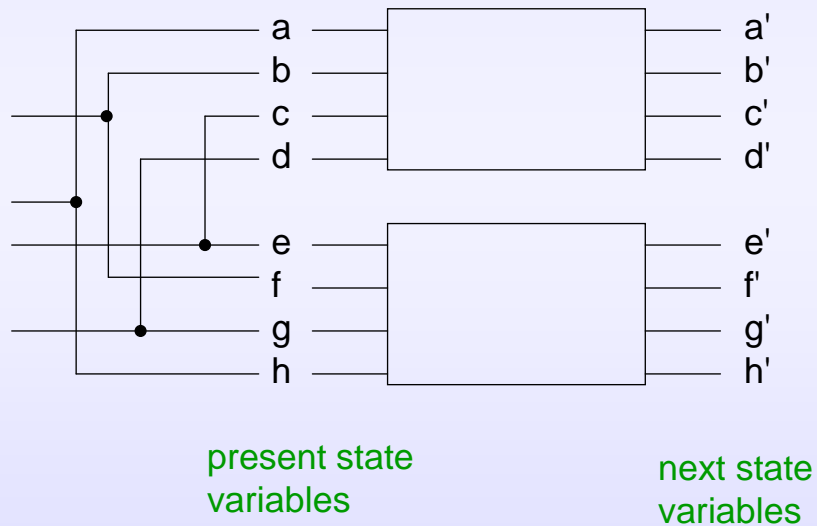

Slide 27

State matching

Basic procedure


Non-equivalence of state variables can be proved by

- analyzing circuit structure
- logic simulation
- SAT (satisfiability solving) or ATPG (automatic test pattern generation)
- BDDs

Slide 28

Equivalence Checking


The "functional paradigm": build canonical representation (e.g. ROBDD, Bryant 86)

 

Slide 29

Equivalence Checking

The SAT-based approach

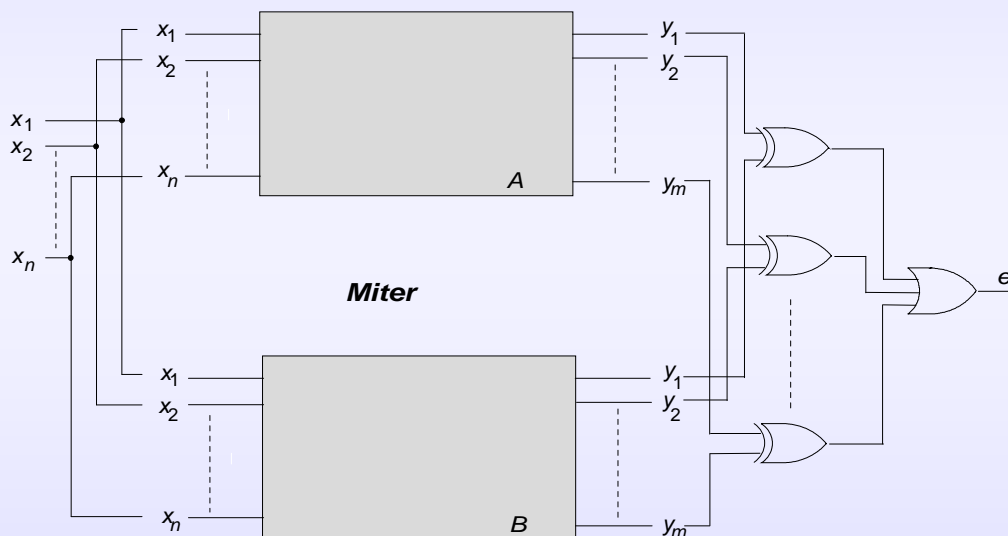

A and B are not equivalent if and only if e is satisfiable.

Slide 30

SAT-solving / ATPG

What problems are hard and what problems are easy?

Stuck-at test generation is easy.

Combinational equivalence checking is hard.

Why?

Source of many problems:

reconvergent fanout causing redundant logic

Slide 31

SAT-solving / ATPG

Combinational stuck-at test generation

- operates on circuit under test (CUT)
- CUT technically makes sense, i.e., redundant structures are fairly local
- problems can be localized by SAT- / ATPG-algorithms

SAT and ATPG work quite robustly!

Slide 32

SAT-solving / ATPG

Combinational equivalence checking


- operates on miter
- miter technically does not make sense
- huge reconvergent fanout structure, if circuits are equivalent miter is a redundant implementation of a constant 0
- problem cannot be localized easily

SAT and ATPG often fail!

Slide 33

Equivalence Checking

 The "**structural paradigm**": exploit structural similarity of designs



Circuits contain internal equivalences

Slide 34

Exploiting internal equivalences



Starting from inputs and moving towards outputs:

- identify equivalences at internal signals in miter
- substitute nodes corresponding to equivalences

Prove/disprove satisfiability of output of modified miter

Slide 35

Example

 
 


circuit partition relevant to determine internal equivalence $d = e$

Local analysis sufficient !



Slide 36

Example

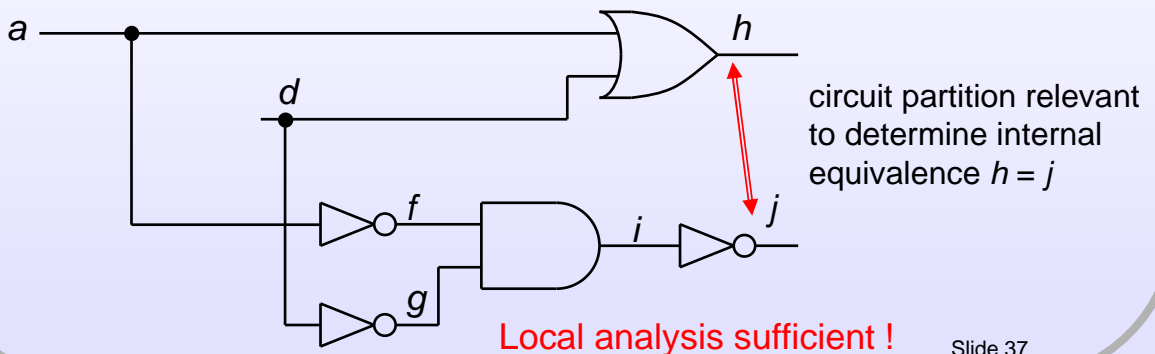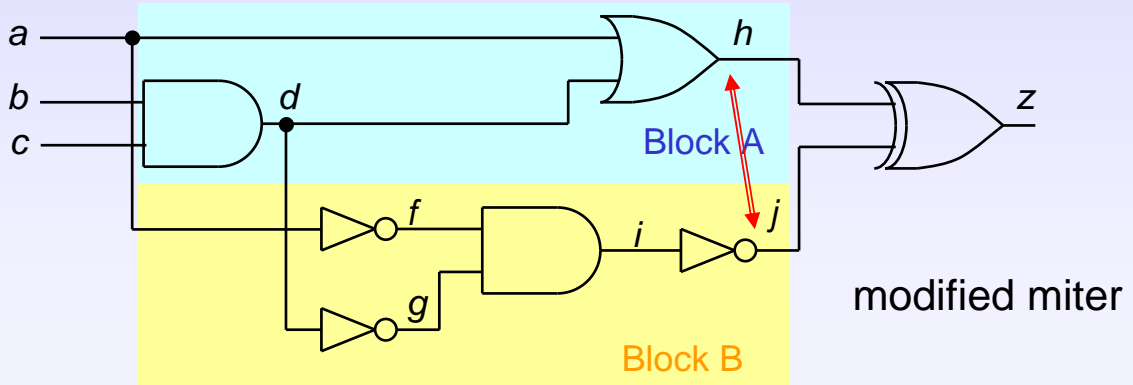

Slide 37

Example

  

Slide 38


Identifying internal equivalences

Methods to identify internal equivalences:

- apply random patterns to determine candidates for equivalent signal pairs, then prove equivalence by SAT or ATPG [Bran93]
- variable probing, implications [Ku93]
- local BDDs for relevant circuit partitions [JaMu95], [Mats96], [KuKr97]


Slide 39

Identifying internal equivalences by SAT

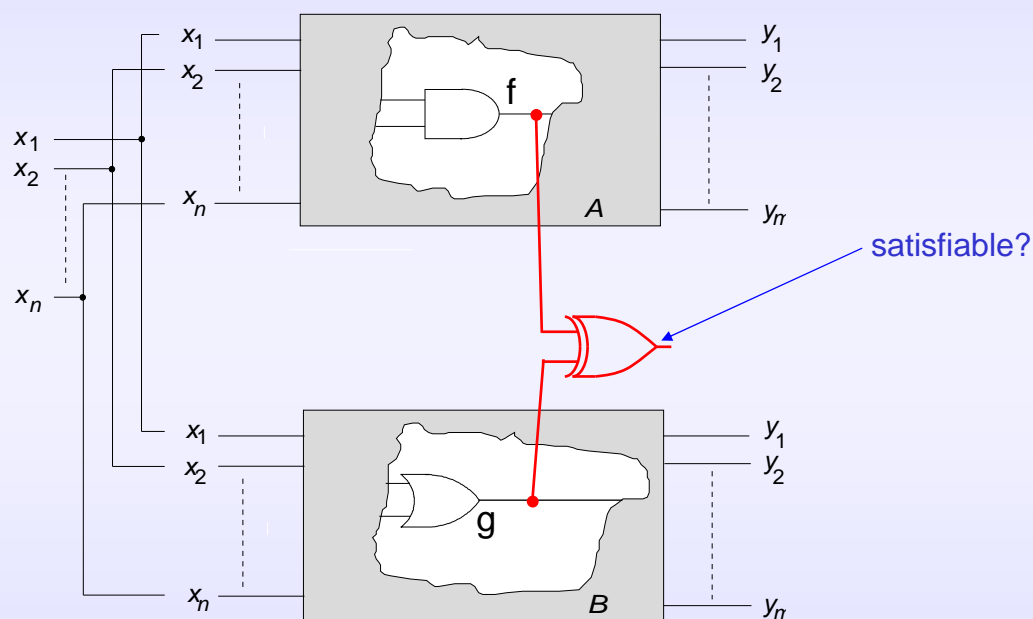

Signals f and g are equivalent if and only if output of XOR is not satisfiable.

Identifying internal equivalences by SAT

 

Slide 41

Identifying internal equivalences by BDDs


Idea: use BDDs restricted to relevant circuit partitions

- determine internal equivalences starting from primary inputs
- use known equivalences as internal "cut points", i.e., as input variables for circuit partitions to be checked for equivalence


Problem: false negatives

Slide 42

Example

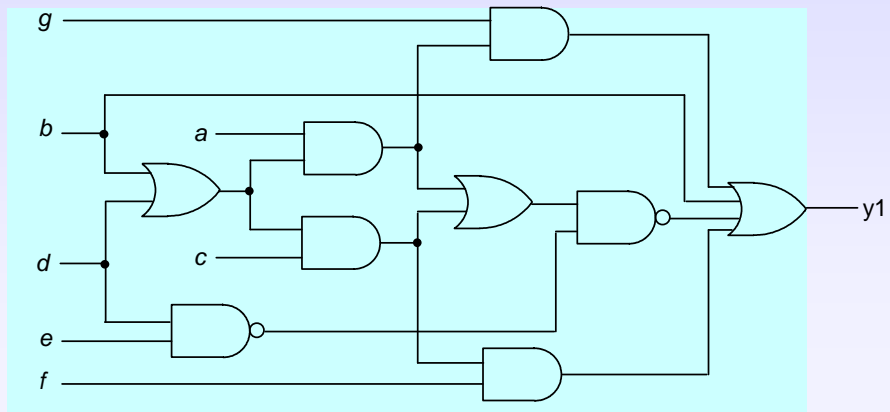


Circuits to
be compared

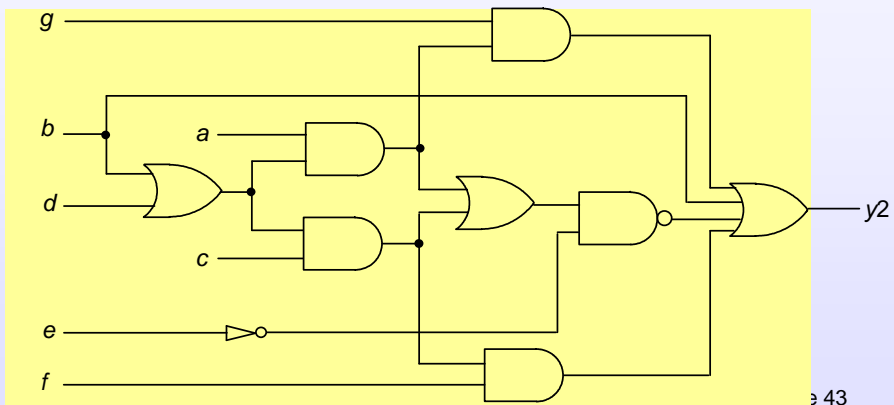

43

Example

Constructing BDDs
for full circuits

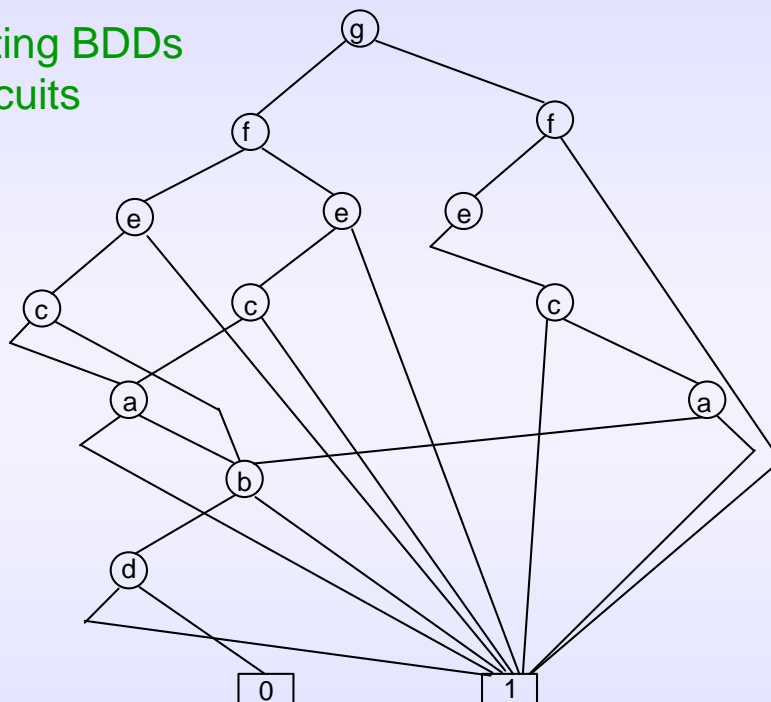


ROBDD for y_1 and y_2 (circuits are equivalent)

Slide 44

Partitioning using internal equivalences

Prove equivalence of C and C' by first proving the equivalence of A and A' and then the equivalence of B and B'

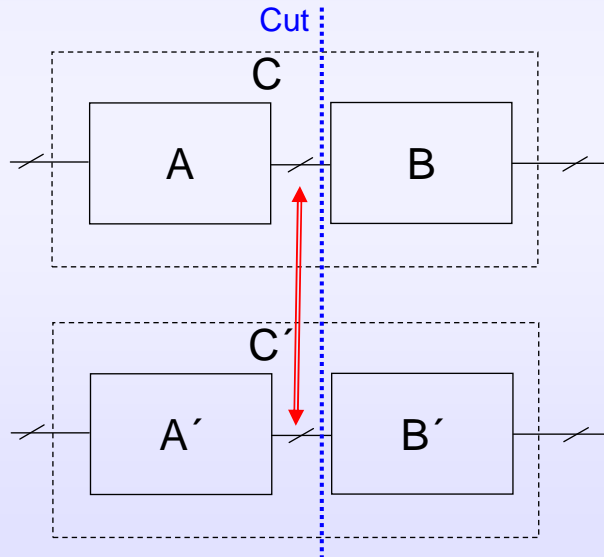


Slide 45

Example



Prove equivalence of eq_1 , eq_2 , eq_3 by building BDDs in terms of primary inputs

Choose cut through circuit, cut line must only contain primary inputs or internal equivalences

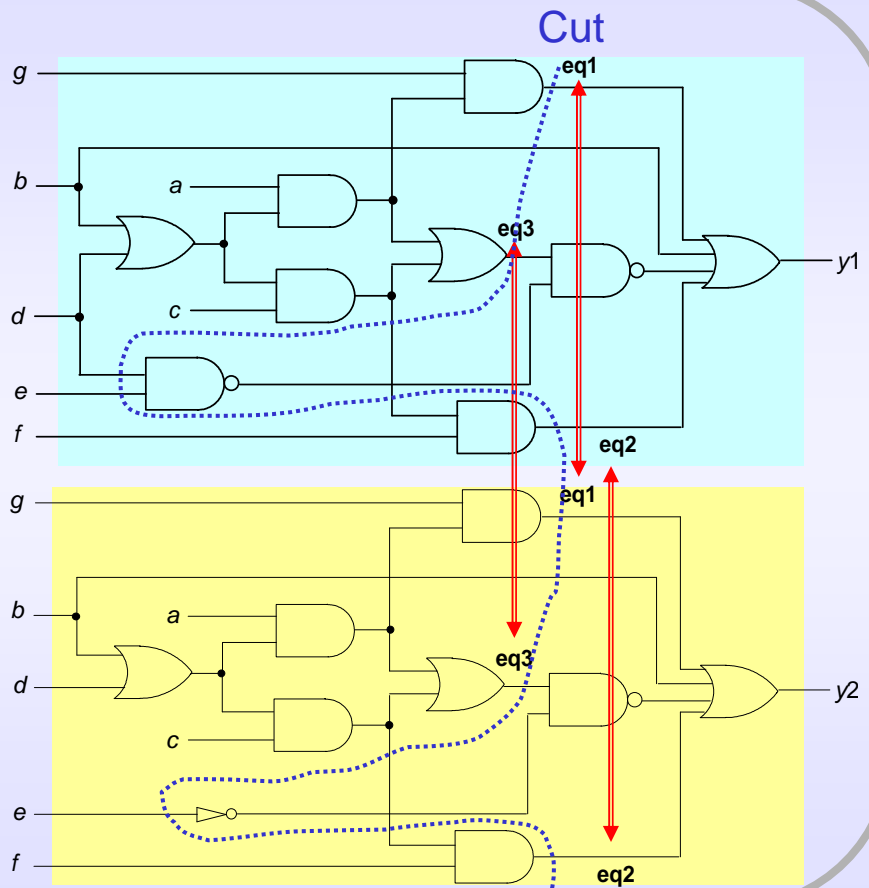Build BDDs for y_1 and y_2 based on cut line




Example

  

BDDs are small

 but not isomorphic
although original
circuits are equivalent!




False negative!

Slide 47

Partitioning using internal equivalences

Note: $C = C'$ and $A = A'$ does not $B = B'$!

Reason: Some combinations of value assignments may not be possible at the cutline (don't cares). For those combinations B and B' can be different without violating $C = C'$.

 


Slide 48

False negatives

Reason: cut points are treated as independent input signals

OBDD for $y_1' \oplus y_2'$

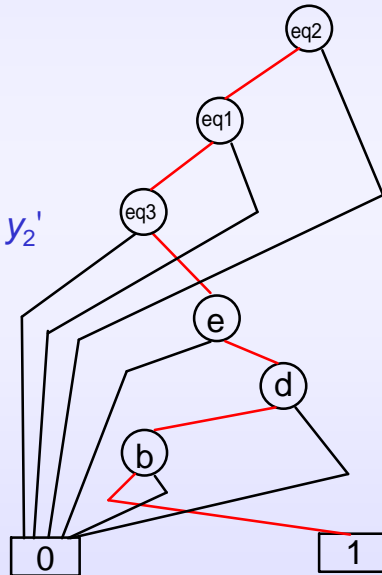


Every path to terminal node 1 corresponds to a (internal) set of value assignments for which the two circuits have different output.

In case of a *false negative* these value assignments are not satisfiable (cannot be justified from the inputs).

Slide 49

Example

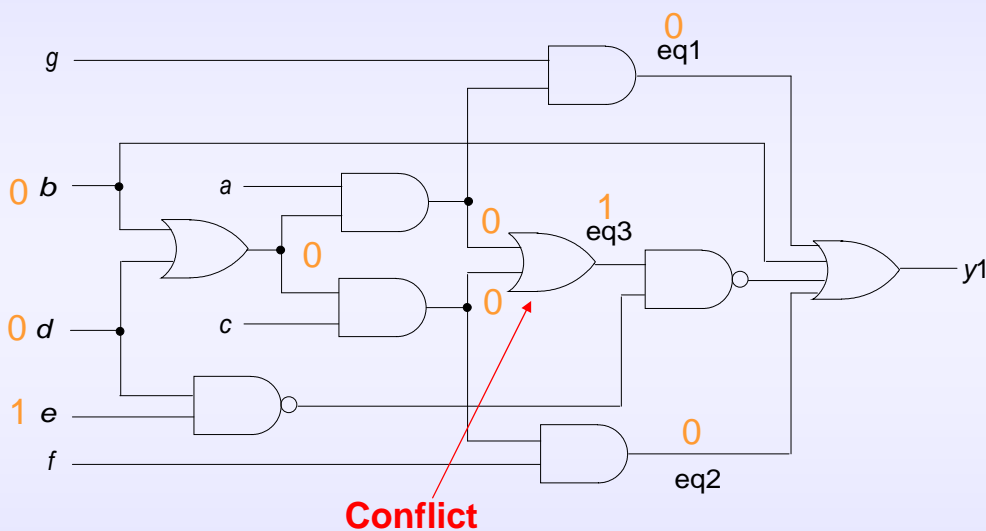

Conflict in original circuit \Rightarrow false negative

Slide 50

Handling false negatives

Techniques:

- explicit satisfiability check of all distinguishing vectors in original circuit [KuPr96]

too complex if many such vectors exist!

- minimize OBDDs by exploiting don't care conditions at cut line [KuPr96]

not exact, also very complex!

Slide 51

Handling false negatives

Techniques (contd.):

- use compose-Operation and move cut line backwards until false negative has disappeared [Mats96]

BDDs may blow up, the right cut line may not be found!

- avoid false negatives right from the beginning by building BDDs for overlapping layers of circuit partitions, overlap creates robustness in case of false negatives [KuKr97]

many BDDs need to be built, right cut might still be missed!

Slide 52

SAT versus BDD

Identifying internal equivalences

SAT-based techniques avoid the false negative problem, circuit does not need to be cut !


BDD-approaches suffer severely from the false negative problem !

But: BDDs are much faster than SAT!

Slide 53

Equivalence checker

Modules

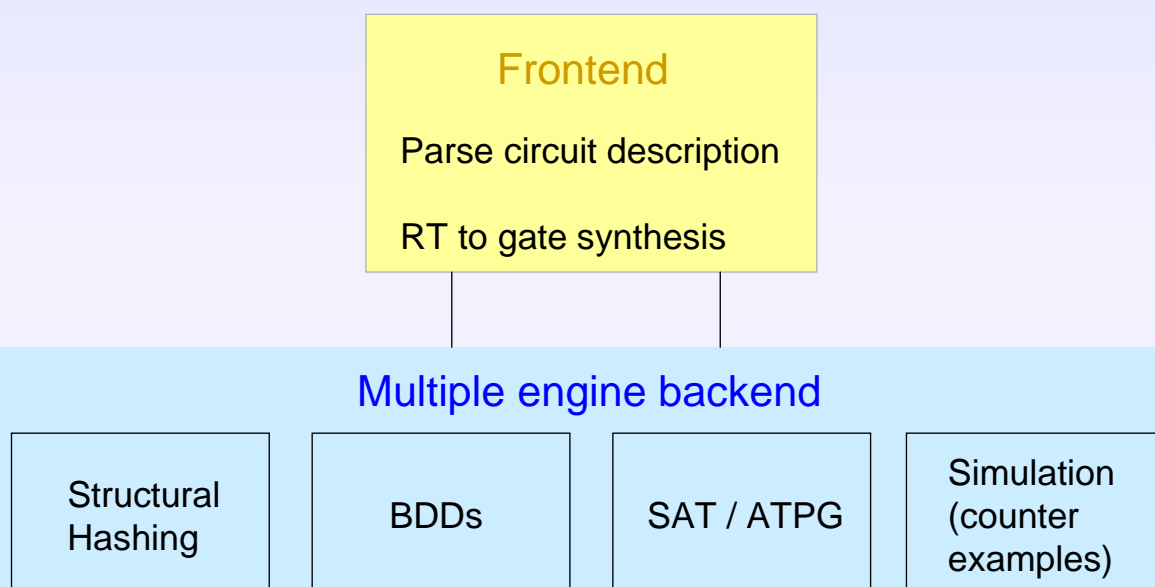

Slide 54

Equivalence Checking

Typical procedure - Example

increasing complexity



represent circuit as combinational netlist of 2-input NAND gates and inverters "*signed AND-graph (SAG)*" [KuKr97]

traverse SAG from inputs to outputs, determine isomorphic sub-graphs and reduce SAG accordingly ("*structure hashing*")

starting at the inputs, determine BDDs for the nodes of the SAG

if two nodes have isomorphic BDDs they are *cut points*, reduce SAG accordingly ("*BDD hashing*"), then use structure hashing for further reduction [KuKr97]

the cut points identified serve as additional variables for the BDDs

Slide 55

Equivalence Checking

Typical procedure - Example (contd.)

increasing complexity



simulate random vectors, counter example?

determine candidates for equivalent node pairs from results of random simulation

check pairs by SAT / ATPG, reduce SAG if equivalence is proved [Bran93], [Ku93]

run SAT / ATPG on the outputs of the miter [KuGa01]

try to build BDD for complete circuit employing sophisticated variable ordering

Interleaving between different steps possible !

Slide 56

Open Problems

Fairly mature technology but some problems remain:

Robust latch mapping for faulty circuits

Equivalence checking for multipliers

Sequential Equivalence Checking

Slide 57

Literature

Combinational Equivalence Checking (1)

- [AaSt94] Aas E. J., Steen T., and Klingsheim K: "Quantifying Design Quality Through Design Experiments", *IEEE Design & Test of Computers*, vol. 11, pp. 27-38, Spring 1994.
- [BeTr89] Berman C. L., and Trevillyan L. H.: "Functional Comparison of Logic Designs for VLSI Circuits", *Proc. Intl. Conf. on Comp.-Aided Design (ICCAD)*, pp. 456-459, 1989.
- [Bran93] Brand D.: "Verification of Large Synthesized Designs", *Proc. IEEE International Conference on Computer-Aided Design (ICCAD)*, Santa Clara, pp. 534-537, Nov. 1993.
- [JaMu95] Jain J., Mukherjee R., and Fujita M.: "Advanced Verification Techniques Based on Learning", *Design Automation Conference (DAC)*, pp. 420 - 426, June 1995.

Slide 58

Literature

Combinational Equivalence Checking (2)

- [KuKr97] Kühlmann A., and Krohm F.: "Equivalence Checking using Cuts and Heaps", *Proc. Design Automation Conference*, San Fransisco, Juni 1997.
- [KuGa01] Kühlmann A., Ganai M., Paruthi V.: "Circuit-based Boolean Reasoning", *Design Automation Conference (DAC)*, pp. 232 - 237, June 2001.
- [Ku93] Kunz W.: "HANNIBAL: An Efficient Tool for Logic Verification Based on Recursive Learning", *Proc. Intl. Conference on Computer-Aided Design (ICCAD)*, Santa Clara, pp. 538-543, Nov. 1993.
- [KuPr96] Kunz W., Pradhan D., and Reddy S.: "A Novel Framework for Logic Verification in a Synthesis Environment", *IEEE Transactions on Computer-Aided Design*, vol. 15, no. 1, pp. 20 - 33, January 1996.

Slide 59

Literature

Combinational Equivalence Checking (3)

- [Mats96] Matsunaga Y.: "An efficient equivalence checker for combinational circuits", *Proc. Design Automation Conference*, pp. 629-634, Las Vegas, 1996.
- [MSGI99] Marquez-Silva J., Glass T.: "Combinational Equivalence Checking Using Satisfiability and Recursive Learning", *Proc. Design, Automation and Test in Europe Conf. (DATE)*, 1999.

Slide 60